

Experimental Competition

I. Determination of Capacitance

Background

It is known that capacitors play a significant role in the electrical circuits. There are several methods of measurements of the capacitance of a capacitor. In this experiment you are required to perform the experiment in order to determine the capacitance of an AC capacitor using a simple electrical circuitry.

In Fig. 1.1 (a), a capacitor of capacitance C and a resistor of resistance R are connected in series to the alternating voltage source of mains frequency. The electrical power which is dissipated at the resistor R depends on the values of \mathcal{E}_0 , C , R and frequency of the mains f . Graphical analysis of this relationship can be used to determine C .

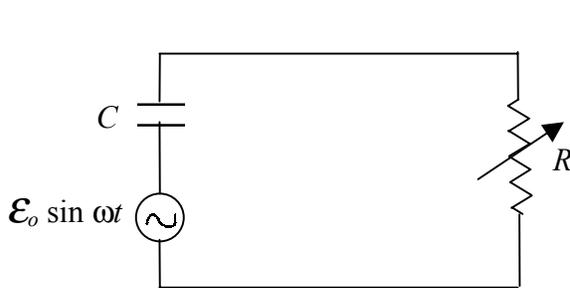


Fig. 1.1 (a): AC Circuit for determination of capacitance C

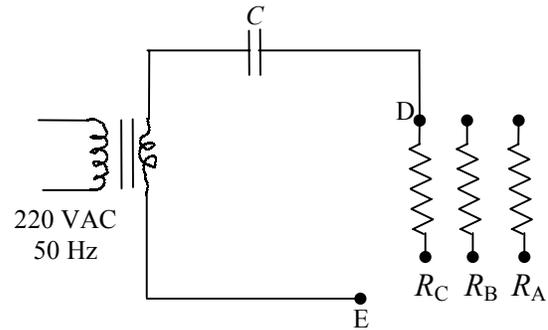


Fig. 1.1 (b): A schematic diagram of the equipment used

Materials and apparatus

1. capacitor
2. three resistors of known values with $\pm 5\%$ errors ($R_A = 680\Omega$, $R_B = 1500\Omega$ and $R_C = 3300\Omega$) as shown in figure 1.1 (b).
3. step-down isolation transformer for alternating voltage source of $f = 50$ Hz
4. digital voltmeter
5. electrical connectors
6. linear graph papers

Warning: The digital multimeter in this experiment will be used for measuring the rms voltage (\tilde{V}) across R only. Do not use it to measure in other modes.

Instructions

- a) Derive the expression for the average power dissipation \bar{P} in resistor R in terms of \mathcal{E}_o , R , C and ω . (1 point)
- b) Deduce the condition for which \bar{P} is a maximum. (1 point)
- c) Convert the dependence found in a) into a linear dependence of certain quantities α and β . (1 point)
- d) Measure the root mean square (effective) voltage V across R for each of all possible combinations of R_A , R_B and R_C . (2.5 points)
- e) Plot \bar{P} versus R and from this graph compute the value of capacitance C . (2 points)
- f) From c), draw the graph of α versus β and determine capacitance C . (2 points)
- g) Estimate the uncertainties in the values of C obtained in e) and f). (0.5 point)
